

Description of Our Design Implementation


- ECE 550 Project Checkpoint4
- Name: Rui Cao, netID: rc384
- Name: Yanxi Li, netID: yl869

1. Overall Design

- Processor: processor.v
 - including steps of The von Neumann Model
 - using dffe.v, control.v, and signExtend.v
- Skeleton: skeleton.v
 - output four clocks (imem_clock, dmem_clock, processor_clock, and regfile_clock)
- PC which outputs the address of instructions in Imem: dffe.v
 - 32-bit DFFE for PC
- Get control signals from instruction machine code : control.v
- Sign-extend module for immediate: signExtend.v
- Clock divider by 4: clock_divider_by2.v
- imem.v and dmem.v
 - generates the dmem and imem files by generating Quartus syncram components
- alu.v and regfile.v
 - provided by Resource folder on Sakai

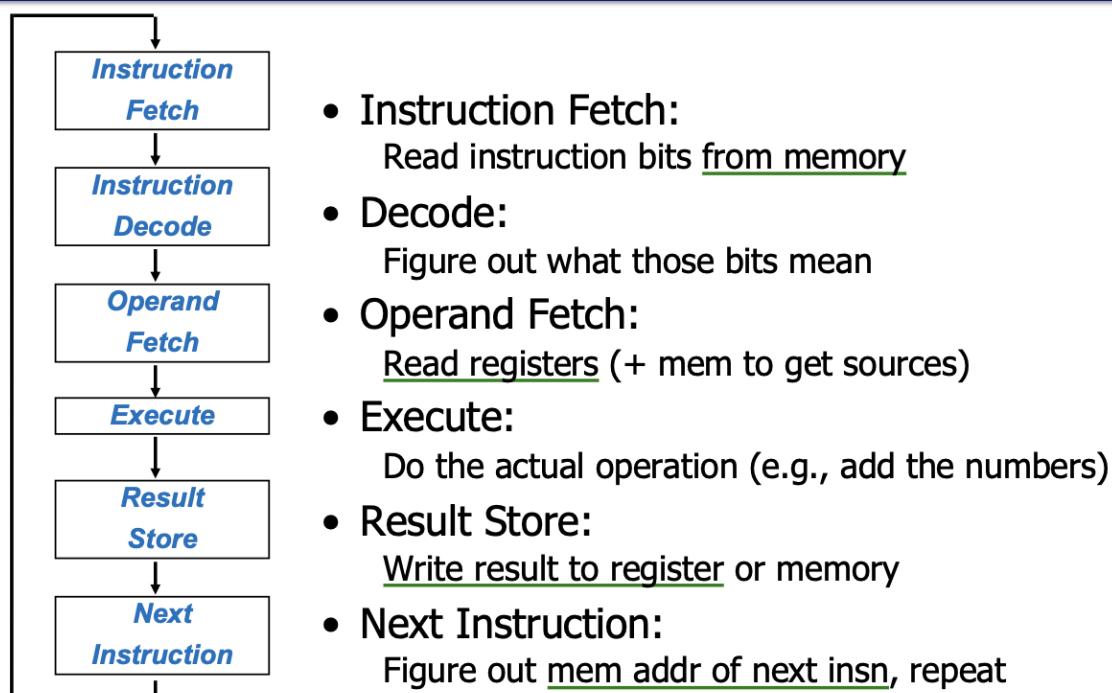2. Detailed Description of Processor

Our processor module is implemented according to steps of The von Neumann Model (the figure below).



2.1. Instruction Fetch:

First, we get the address of instructions in Imem from 32-bit DFFE (32-bit PC).
 Second, compute the address of the next instruction (adding 1) using alu module.
 Third, get the instruction address in Imem (address_imem) from the first 12 bits of 32-bit PC.

2.2. Instruction Decode:


- According to the Instruction Machine Code Format of PDF, figure out what those bits in Instruction Machine Code (q_imem) mean.

| Instruction Type | Instruction Format | | | | | | | | | | | | | |
|-------------------|-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|------------------|-------------------------|-----------------|-----------------|-----------------|--|-------------------|----------------------|------------------|-------------------------|-----------------|-----------------|-----------------|
| R | <table><tr><td>Opcode [31:27]</td><td>\$rd [26:22]</td><td>\$rs [21:17]</td><td>\$rt [16:12]</td><td>shamt [11:7]</td><td>ALU op [6:2]</td><td>Zeroes [1:0]</td></tr></table> | | | | | | | Opcode [31:27] | \$rd [26:22] | \$rs [21:17] | \$rt [16:12] | shamt [11:7] | ALU op [6:2] | Zeroes [1:0] |
| Opcode [31:27] | \$rd [26:22] | \$rs [21:17] | \$rt [16:12] | shamt [11:7] | ALU op [6:2] | Zeroes [1:0] | | | | | | | | |
| I | <table><tr><td>Opcode [31:27]</td><td>\$rd [26:22]</td><td>\$rs [21:17]</td><td colspan="4">Immediate (N) [16:0]</td></tr></table> | | | | | | | Opcode [31:27] | \$rd [26:22] | \$rs [21:17] | Immediate (N) [16:0] | | | |
| Opcode [31:27] | \$rd [26:22] | \$rs [21:17] | Immediate (N) [16:0] | | | | | | | | | | | |
| JJ | <table><tr><td>Opcode [31:27]</td><td colspan="6">Target (T) [26:0]</td></tr></table> | | | | | | | Opcode [31:27] | Target (T) [26:0] | | | | | |
| Opcode [31:27] | Target (T) [26:0] | | | | | | | | | | | | | |
| JII | <table><tr><td>Opcode [31:27]</td><td>\$rd [26:22]</td><td colspan="5">Zeroes [21:0]</td></tr></table> | | | | | | | Opcode [31:27] | \$rd [26:22] | Zeroes [21:0] | | | | |
| Opcode [31:27] | \$rd [26:22] | Zeroes [21:0] | | | | | | | | | | | | |

- Besides, r30 (rstatus) is \$30.

 2.3. Control Circuit (using control.v):


- We implement control circuit using "Random Logic" provided by our PPT 07 Page 29 (as shown in the figure below).



29

- First, get 1-bit typeR (whether this instruction is type R or not) using 5-bit opcode and AND gate. The same method is used for isAddi, isSw, isLw. Second, get 1-bit isAdd and isSub using 5-bit aluOp, 1-bit typeR, and AND gate. Third,

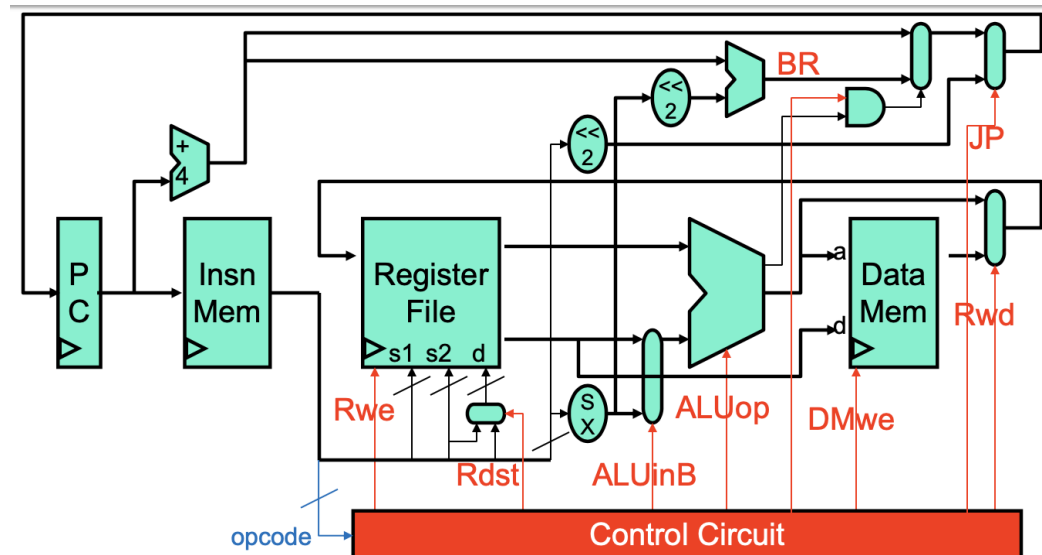The usage of each control signal is shown in the figure below (The following steps will use them).



2.4. Operand Fetch:

- According to datapath of our PPT 07, the output ctrl_readRegA is always rs for these instructions in this Checkpoint. But, for the output ctrl_readRegB, if the instruction is sw, it's rd; otherwise, it's rt.

2.5. Execution (using alu.v and signExtend.v):

- 17-bit immediate will become 32-bit after using signExtend module.
data_operandA is directly the input data_readRegA, while data_operandB depends on the control signal ALUinB and it is either 32-bit immediate or the input data_readRegB.
- Besides, ctrl_ALUopcode depends on whether the instruction is type R.

2.5. Result Store:

- Write result to register:
 - The output `ctrl_writeEnable` is the control signal `Rwe`.
 - Note: overflow will affect `ctrl_writeReg` and `data_writeReg`. If overflow occurs, `ctrl_writeReg` will be `r30`; otherwise, it is `rd`.
 - When the instruction is `lw`, `data_writeReg` is the output of `dmem` (`q_dmem`).
- Write result to memory:
 - The data which is written to `dmem` is `data_readRegB`.
 - The output `wren` is the control signal `DMwe`.