

Description of Our Design Implementation


- ECE 550 Project Checkpoint5
- Name: Rui Cao, netID: rc384
- Name: Yanxin Li, netID: yl869

1. Overall Design

- The overall design is consistent with checkpoint 4. Compared with checkpoint 4, only the implementation of 7 additional instructions in processor.v and some control signals have been added in control.v.
- Processor: processor.v
 - including steps of The von Neumann Model
 - using dffe.v, control.v, and signExtend.v
- Skeleton: skeleton.v
 - output four clocks (imem_clock, dmem_clock, processor_clock, and regfile_clock)
- PC which outputs the address of instructions in Imem: dffe.v
 - 32-bit DFFE for PC
- Get control signals from instruction machine code : control.v
- Sign-extend module for immediate: signExtend.v
- Clock divider by 4: clock_divider_by2.v
- imem.v and dmem.v
 - generates the dmem and imem files by generating Quartus syncram components
- alu.v and regfile.v
 - provided by Resource folder on Sakai

 2. Detailed Description of Processor

Our processor module is implemented according to steps of The von Neumann Model (the figure below).



- **Instruction Fetch:**
Read instruction bits from memory
- **Decode:**
Figure out what those bits mean
- **Operand Fetch:**
Read registers (+ mem to get sources)
- **Execute:**
Do the actual operation (e.g., add the numbers)
- **Result Store:**
Write result to register or memory
- **Next Instruction:**
Figure out mem addr of next insn, repeat

2.1. Instruction Fetch:

- First, we get the address of instructions in Imem from 32-bit DFFE (32-bit PC).
- Second, compute the address of the next instruction.
 - PC + 1
 - or T: jal T or bex T (& \$rstatus != 0) or j T
 - or PC + 1 + N: bne \$rd, \$rs, N (& \$rd != \$rs) or blt \$rd, \$rs, N (& \$rd < \$rs)
 - or \$rd: jr \$rd
- Third, get the instruction address in Imem (address_imem) from the first 12 bits of 32-bit PC.

2.2. Instruction Decode:


- According to the Instruction Machine Code Format of PDF, figure out what those bits in Instruction Machine Code (q_imem) mean.

Instruction Type	Instruction Format													
R	<table><tr><td>Opcode [31:27]</td><td>\$rd [26:22]</td><td>\$rs [21:17]</td><td>\$rt [16:12]</td><td>shamt [11:7]</td><td>ALU op [6:2]</td><td>Zeroes [1:0]</td></tr></table>							Opcode [31:27]	\$rd [26:22]	\$rs [21:17]	\$rt [16:12]	shamt [11:7]	ALU op [6:2]	Zeroes [1:0]
Opcode [31:27]	\$rd [26:22]	\$rs [21:17]	\$rt [16:12]	shamt [11:7]	ALU op [6:2]	Zeroes [1:0]								
I	<table><tr><td>Opcode [31:27]</td><td>\$rd [26:22]</td><td>\$rs [21:17]</td><td colspan="4">Immediate (N) [16:0]</td></tr></table>							Opcode [31:27]	\$rd [26:22]	\$rs [21:17]	Immediate (N) [16:0]			
Opcode [31:27]	\$rd [26:22]	\$rs [21:17]	Immediate (N) [16:0]											
JI	<table><tr><td>Opcode [31:27]</td><td colspan="6">Target (T) [26:0]</td></tr></table>							Opcode [31:27]	Target (T) [26:0]					
Opcode [31:27]	Target (T) [26:0]													
JII	<table><tr><td>Opcode [31:27]</td><td>\$rd [26:22]</td><td colspan="5">Zeroes [21:0]</td></tr></table>							Opcode [31:27]	\$rd [26:22]	Zeroes [21:0]				
Opcode [31:27]	\$rd [26:22]	Zeroes [21:0]												

- Besides, r30 (rstatus) is \$30. r0 is \$0. r31 is \$31

 2.3. Control Circuit (using control.v):

- We implement control circuit using "Random Logic" provided by our PPT 07 Page 29 (as shown in the figure below).



29

- First, get 1-bit typeR (whether this instruction is type R or not) using 5-bit opcode and AND gate. The same method is used for isAddi, isSw, isLw, isJ, isJal, isBlt, isBne, isJr, isSetx. Second, get 1-bit isAdd and isSub using 5-bit aluOp, 1-bit typeR, and AND gate. Third, get control signals, such as Rwe, DMwe, and Rdst, using results obtained above and OR gate.
- The usage of each control signal is shown in the figure below (The following steps will use them).

- Write result to register:
 - The output `ctrl_writeEnable` is the control signal `Rwe`.
 - Note: overflow will affect `ctrl_writeReg` and `data_writeReg`. If overflow occurs, `ctrl_writeReg` will be `r30`. `ctrl_writeReg`:
 - `$rd`
 - or `$r30`: overflow or `setx`
 - or `$r31`: `jal`
 - When the instruction is `lw`, `data_writeReg` is the output of `dmem` (`q_dmem`). `data_writeReg`:
 - overflow data: 1 or 2 or 3
 - or `data_result` from `alu`
 - or `q_dmem`: `lw`
 - or `T`: `setx`

- or PC + 1: jal
- Write result to memory:
 - The data which is written to dmem is data_readRegB.
 - The output wren is the control signal DMwe.